

$$\underline{U}_L = j \cdot X_L \cdot \underline{I}$$

$$\underline{U}_C = -j \cdot X_C \cdot \underline{I}$$

$$\underline{U}_R = R \cdot \underline{I}$$

$$X_L = \omega \cdot L \quad \frac{1}{j} = -j$$

$$X_C = \frac{1}{\omega C} \quad \frac{1}{-j} = j$$

$$\underline{U} = \underline{Z} \cdot \underline{I}$$

Ohm's law for AC circuit


$$\underline{I} = \underline{U} \cdot \underline{Y}$$

Inverse Ohm's law for AC circuit

$$\underline{u} = U \cdot e^{j\varphi_u}$$

$$\underline{i} = I \cdot e^{j\varphi_i}$$

$$\underline{z} = Z \cdot e^{j\varphi}$$

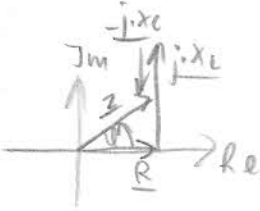


\underline{Z} - impedance

\underline{Y} - admittance

$$\underline{Y} = \frac{1}{\underline{Z}} \text{ [S]}$$

$$j^2 = -1$$

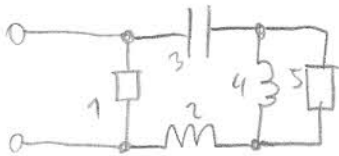Designate total impedance of circuit shown below:



$$z_k = 1 \quad (k=1,2,3,4,5)$$

$$\underline{z}_1 = 1 \text{ [}\Omega\text{]}$$

$$\underline{z}_2 = j \text{ [}\Omega\text{]}$$

$$\underline{z}_3 = -j \text{ [}\Omega\text{]}$$

$$\underline{z}_4 = j \text{ [}\Omega\text{]}$$

$$\underline{z}_5 = 1 \text{ [}\Omega\text{]}$$

$$\underline{Y}_{45} = \underline{Y}_4 + \underline{Y}_5 = \frac{1}{j} + \frac{1}{1} = -j + 1 = 1 - j$$

$$\underline{z}_{234} = \underline{z}_2 + \underline{z}_3 + \frac{1}{\underline{Y}_{45}} = j - j + \frac{1}{1 - j} = \frac{1(1+j)}{(1-j)(1+j)} = \frac{1+j}{1-j-j+1}$$

$$\underline{z}_{234} = \frac{1+j}{2}$$

$$\underline{Y}_{12345} = \underline{Y}_1 + \frac{1}{\underline{z}_{2345}} = 1 + \frac{1}{\frac{1+j}{2}} = 1 + \frac{2}{1+j} = 1 + \frac{2(1-j)}{(1+j)(1-j)} = 1 + \frac{2(1-j)}{1-j-j+1}$$

$$\underline{Y}_{12345} = 1 + \frac{2(1-j)}{2} = 1 + 1 - j = 2 - j \text{ [S]}$$

$$\underline{z}_{12345} = \frac{1}{\underline{Y}_{12345}} = \frac{1}{2-j} = \frac{2+j}{(2-j)(2+j)} = \frac{2+j}{4-2j+2j+1} = \frac{2+j}{5} \text{ [}\Omega\text{]}$$

$$\underline{z}_{12345} = \frac{1}{5} \cdot (2+j) \text{ [}\Omega\text{]}$$