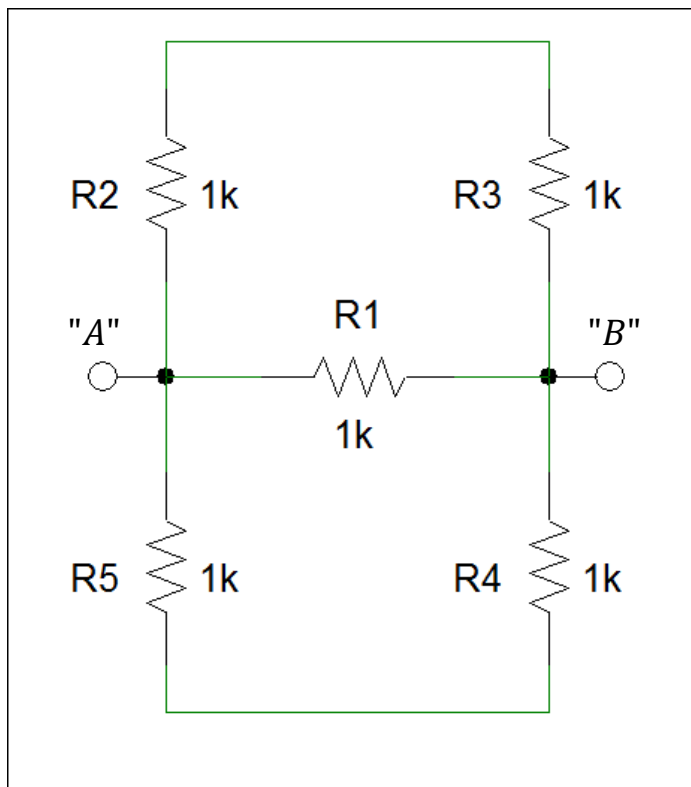


Total resistance of electric DC circuit

Total resistance of electrical circuit will be calculated. Total resistance is seen from terminals *A* i *B*. Before starting calculations types of connections between resistors will be analyzed.



Drawing 1. Electrical circuit.

Resistors *R2* and *R3* are connected in series. They will be replaced with resistance *R23*.

$$R_{23} = R_2 + R_3$$

$$R_{23} = 1000 + 1000$$

$$R_{23} = 2000[\Omega]$$

$$R_{23} = 2[k\Omega]$$

Resistors *R4* and *R5* are connected in series. They will be replaced with resistance *R45*.

$$R_{45} = R_4 + R_5$$

$$R_{45} = 1000 + 1000$$

$$R_{45} = 2000[\Omega] = 2[k\Omega]$$

Resistor *R1* is connected in parallel with resistances *R23* i *R45*. Relation between resistance *R* and conductance *G* will be applied $\rightarrow G = \frac{1}{R}$.

$$G_1 = \frac{1}{R_1} = \frac{1}{1000} [S]$$

$$G_{23} = \frac{1}{R_{23}} = \frac{1}{2000} [S]$$

$$G_{45} = \frac{1}{R_{45}} = \frac{1}{2000} [S]$$

$$G_{12345} = G_1 + G_{23} + G_{45}$$

$$G_{12345} = \frac{1}{1000} + \frac{1}{2000} + \frac{1}{2000} = \frac{2}{2000} + \frac{1}{2000} + \frac{1}{2000}$$

$$G_{12345} = \frac{4}{2000} [S]$$

Resistance which is seen from *A* and *B* terminals, is given by equation below.

$$R_{AB} = \frac{1}{G_{12345}}$$

$$R_{AB} = \frac{2000}{4}$$

$$R_{AB} = 250[\Omega]$$