

Application of branch current method to solve AC circuit.

In this example branch current method will be used to solve electric AC circuit. Example AC circuit is specific because it is a model of one phase from electric AC three phase motor.

Number of nodes we mark as n , number of equations for Kirchhoff's current law is equal to $(n - 1)$.

$$KCL \rightarrow (n - 1)$$


Number of Kirchhoff's voltage law equations depends from number branches and nodes in circuit. General formula for number of Kirchhoff's voltage law equations is given by formula:

$$KVL \rightarrow m - (n - 1)$$

where:

m – number of branches

n – number of nodes

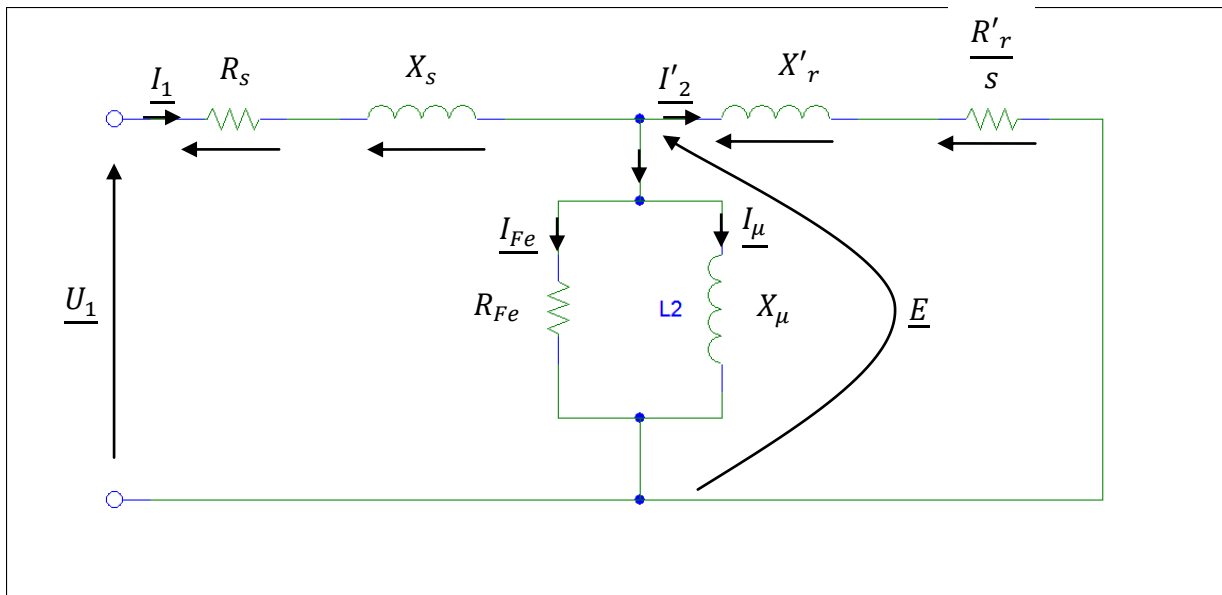

Drawing 1. Calculation model of one phase of three phase AC motor.

where:

\underline{U}_1 → supply voltage's vector of AC motor's one phase

\underline{I}_1 → current of one stator's one phase

R_s → stator's resistance

X_s → stator's inductive reactance

\underline{I}'_2 → current of one rotor's phase which is brought to stator

X'_r → inductive reactance rotor's phase which is brought to stator

$\frac{R'_r}{s}$ → resistance of rotor's phase divided by slip which is brought to stator

$s = \frac{n_0 - n}{n_0}$ → rotor's slip

\underline{E} → electromotorical force

\underline{I}_{Fe} → current which represents losses in iron

R_{Fe} → resistance of iron

\underline{I}_{μ} → magnetizing current

X_{μ} → magnetizing inductive reactance

Kirchhoff's current law (KCL) equation for circuit:

$$\underline{I}_1 - \underline{I}'_2 - \underline{I}_{Fe} - \underline{I}_{\mu} = 0$$

Kirchhoff's voltage law (KVL) equation for first mesh:

$$\underline{U}_1 - R_s \cdot \underline{I}_1 - j \cdot X_s \cdot \underline{I}_1 - \underline{E} = 0$$

Kirchhoff's voltage law (KVL) equation for second mesh:

$$\underline{E} - j \cdot X'_r \cdot \underline{I}'_2 - \frac{R'_r}{s} \cdot \underline{I}'_2 = 0$$

Note also that

$$\underline{E} = R_{Fe} \cdot \underline{I}_{Fe} = j \cdot X_{\mu} \cdot \underline{I}_{\mu}$$