

Application of branch current method to AC circuit.

In this example we will consider electric AC circuit. Branch current method will be applied for calculation of currents in circuit.


$$\underline{E} = 10[V] = 10 \cdot e^{j \cdot 0}[V]$$

$$\underline{I} = 1 - j \cdot 1[A] = \sqrt{1^2 + 1^2} \cdot e^{-j \cdot \frac{\pi}{4}}[A] = \sqrt{2} \cdot e^{-j \cdot \frac{\pi}{4}}[A]$$

$$|Z_{L1}| = 1[\Omega] \rightarrow Z_{L1} = j[\Omega]$$

$$|Z_{C1}| = 2[\Omega] \rightarrow Z_{C1} = -j \cdot 2[\Omega]$$

$$|Z_{R1}| = 3[\Omega] \rightarrow Z_{R1} = 3[\Omega]$$

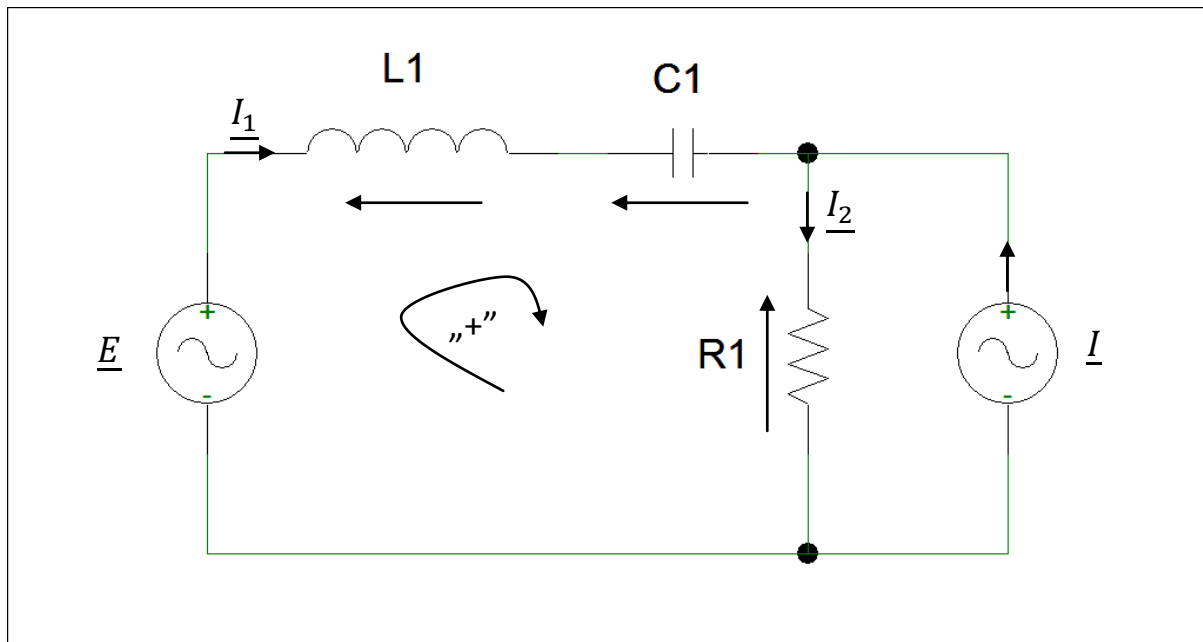

Drawing 1. Electrical AC circuit.

Kirchhoff's current law equation (KCL)

$$\underline{I}_1 + \underline{I} - \underline{I}_2 = 0$$

Kirchhoff's voltage law equation (KVL)

$$\underline{E} - \underline{I}_1 \cdot \underline{Z}_{L1} - \underline{I}_1 \cdot \underline{Z}_{C1} - \underline{I}_2 \cdot \underline{Z}_{R1} = 0$$

$$\underline{I}_2 = \underline{I}_1 + \underline{I}$$

$$\underline{E} - \underline{I}_1 \cdot \underline{Z}_{L1} - \underline{I}_1 \cdot \underline{Z}_{C1} - (\underline{I}_1 + \underline{I}) \cdot \underline{Z}_{R1} = 0$$

$$\underline{E} - \underline{I}_1 \cdot \underline{Z}_{L1} - \underline{I}_1 \cdot \underline{Z}_{C1} - \underline{I}_1 \cdot \underline{Z}_{R1} - \underline{I} \cdot \underline{Z}_{R1} = 0$$

$$\underline{E} - \underline{I}_1 \cdot (\underline{Z}_{L1} + \underline{Z}_{C1} + \underline{Z}_{R1}) - \underline{I} \cdot \underline{Z}_{R1} = 0$$

$$\underline{I}_1 = \frac{\underline{E} - \underline{I} \cdot \underline{Z}_{R1}}{\underline{Z}_{L1} + \underline{Z}_{C1} + \underline{Z}_{R1}}$$

$$\underline{I}_1 = \frac{10 - \sqrt{2} \cdot e^{-j \cdot \frac{\pi}{4}} \cdot 3}{j - j \cdot 2 + 3}$$

$$\underline{I}_1 = \frac{10 - \sqrt{2} \cdot e^{-j \cdot \frac{\pi}{4}} \cdot 3}{3 - j}$$

$$\underline{I}_1 = \frac{10 - \sqrt{2} \cdot e^{-j \cdot \frac{\pi}{4}} \cdot 3}{3 - j} \cdot \frac{3 + j}{3 + j} = \frac{10 - 3 \cdot (1 - j)}{3 - j} \cdot \frac{3 + j}{3 + j}; \text{ where } j^2 = -1$$

$$\underline{I}_1 = \frac{10 - 3 - j \cdot 3}{3 - j} \cdot \frac{3 + j}{3 + j} = \frac{7 - j \cdot 3}{3 - j} \cdot \frac{3 + j}{3 + j}$$

$$\underline{I}_1 = \frac{21 + j \cdot 7 - j \cdot 9 - 3 \cdot (-1)}{9 + j \cdot 3 - j \cdot 3 + 1} = \frac{21 - j \cdot 2 + 3}{10}$$

$$\underline{I}_1 = \frac{24}{10} - j \cdot \frac{2}{10} [A]$$

$$I_1 = \sqrt{\left(\frac{24}{10}\right)^2 + \left(\frac{2}{10}\right)^2} = 2,40 [A]$$

$$\underline{I}_2 = \underline{I}_1 + \underline{I}$$

$$\underline{I}_2 = \frac{24}{10} - j \cdot \frac{2}{10} + 1 - j$$

$$\underline{I}_2 = \frac{34}{10} - j \cdot \frac{12}{10}$$

$$I_2 = \sqrt{\left(\frac{34}{10}\right)^2 + \left(\frac{12}{10}\right)^2} = 3,61 [A]$$