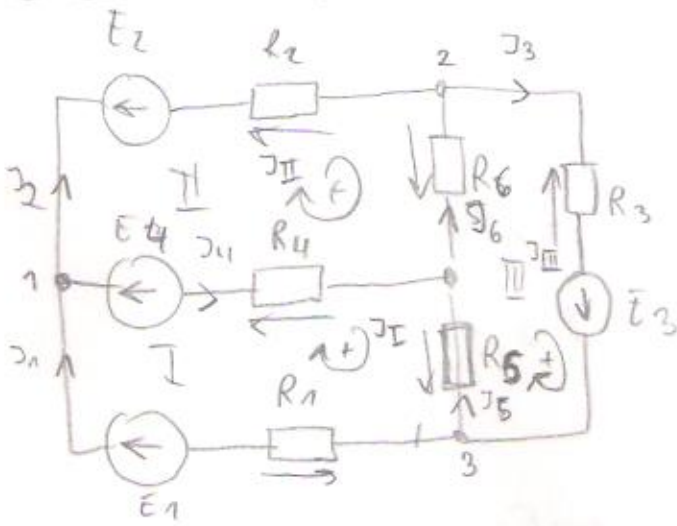


Mesh current method - derivation



$$\begin{aligned} & I_k (n-1) \\ & II_k (m-(n-1)) \end{aligned}$$

$$I_k \quad n-1 \quad 4-1=3$$

Currents of internal branches are expressed by currents of external branches

node 1

$$J_1 - J_2 - J_4 = 0 \Rightarrow J_4 = J_1 - J_2$$

node 2

$$J_2 + J_6 - J_3 = 0 \Rightarrow J_6 = J_3 - J_2$$

node 3

$$J_3 - J_5 - J_1 = 0 \Rightarrow J_5 = J_3 - J_1$$

$$II_k \quad m-(n-1) \quad 6-3=3$$

mesh I

$$-J_1 R_1 + E_1 - E_4 - J_4 R_4 + J_5 R_5 = 0$$

mesh II

$$J_4 R_4 + E_4 - E_2 - J_2 R_2 + J_6 R_6 = 0$$

mesh III

$$-J_5 R_5 - J_6 R_6 - J_3 R_3 + E_3 = 0$$

External branches currents will be substituted as internal branches currents. Expressions for internal currents will be used.

mesh I

$$-J_1 R_1 + E_1 - E_4 - (J_1 - J_2) R_4 + (J_3 - J_1) R_5 = 0$$

$$-J_1 R_1 - J_1 R_4 + J_2 R_4 + J_3 R_5 - J_1 R_5 = E_4 - E_1$$

$$-J_1 (R_1 + R_4 + R_5) + J_2 R_4 + J_3 R_5 = E_4 - E_1$$

$$J_1 (R_1 + R_4 + R_5) - J_2 R_4 - J_3 R_5 = E_1 - E_4$$

J_I

$$J_1 \cdot R_{11} - J_2 \cdot R_{12} - J_3 \cdot R_{13}$$

$$J_I (R_{11} + R_4 + R_5) - J_{II} R_4 - J_{III} R_5 = E_1 - E_4$$

mesh equation for mesh I

mesh II

External branches currents will be substituted as internal branches currents. Expressions for internal currents will be used.

$$J_4 R_4 + E_4 - E_2 - J_2 R_2 + J_6 R_6 = 0$$

$$(J_1 - J_2) R_4 + E_4 - E_2 - J_2 R_2 + (J_3 - J_2) R_6 = 0$$

$$J_1 R_4 - J_2 R_4 - J_2 R_2 + J_3 R_6 - J_2 R_6 = -E_4 + E_2$$

$$-J_2 (R_2 + R_4 + R_6) + J_1 R_4 + J_3 R_6 = -E_4 + E_2$$

$$J_2 \underbrace{(R_2 + R_4 + R_6)}_{R_{22}} - \underbrace{J_1 R_4}_{R_{21}} - \underbrace{J_3 R_6}_{R_{23}} = E_4 - E_2$$

$$J_{II} \cdot (R_2 + R_4 + R_6) - J_I \cdot R_4 - J_{III} \cdot R_6 = E_4 - E_2 \quad \text{mesh equation for mesh II}$$

mesh III

$$-J_5 R_5 - J_6 R_6 - J_3 R_3 + E_3 = 0$$

$$-(J_3 - J_1) R_5 - (J_3 - J_2) R_6 - J_3 R_3 + E_3 = 0$$

$$-J_3 R_5 + J_1 R_5 - J_3 R_6 + J_2 R_6 - J_3 R_3 = -E_3$$

$$J_3 R_5 + J_3 R_6 + J_3 R_3 - J_1 R_5 - J_2 R_6 = E_3$$

$$J_3 \underbrace{(R_3 + R_5 + R_6)}_{R_{33}} - \underbrace{J_1 R_5}_{R_{31}} - \underbrace{J_2 R_6}_{R_{32}} = E_3$$

$$J_{III} (R_3 + R_5 + R_6) - J_I R_5 - J_{II} R_6 = E_3 \quad \text{mesh equation for mesh III}$$

$$J_1 = J_I$$


$$J_4 = J_I - J_{II}$$

$$J_2 = J_{II}$$

$$J_5 = J_{III} - J_I$$

$$J_3 = J_{III}$$

$$J_6 = J_{III} - J_{II}$$

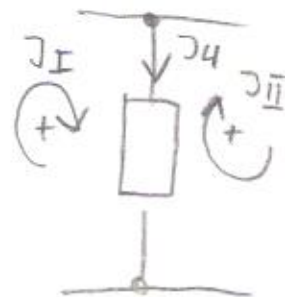

$$J_4 = J_I - J_{II}$$