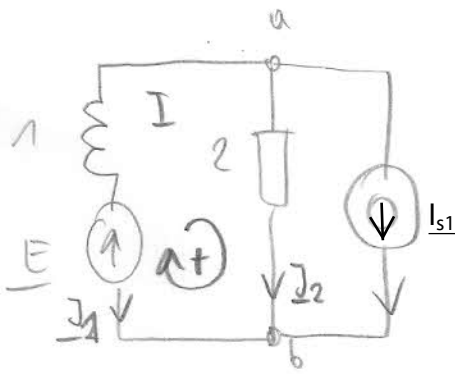


Calculate currents in branches using node-voltage method and mesh current method.



Known:  
 $Z_1 = Z_2 = 1 [\text{Ohm}]$   
 $E_1 = 100 [\text{V}]$   
 $I_{s1} = -j10 [\text{A}]$   
 $n = 2$   
 $m = 2$

Current source is not a branch  
 $n$  - number of nodes  
 $m$  - number of branches

Node method uses Kirchhoff's current law (KCL). Node method does not see voltage sources. Physical voltage sources are transformed to virtual current source  $E \rightarrow I_s'$ . In this method we also have to assume that one of nodes has potential 0[V].

Number of equations for the Kirchhoff's current law is given by formula:

equations for KCL =  $n - 1$

$n - 1 = 2 - 1 = 1$


$$Z_1 = j \quad Y_1 = \frac{1}{j} = -j$$

$$Z_2 = 1 \quad Y_2 = 1$$

Assumption  $V_b = 0 [\text{V}]$

Contraction
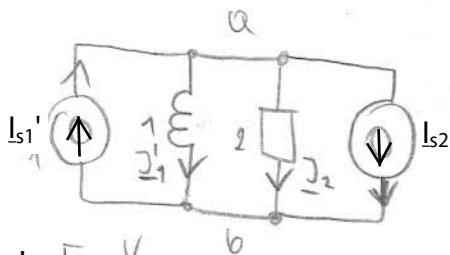
$$\left( \sum I_s \right)_a = E_1 \cdot Y_1 - I_{s2} = V_a (Y_1 + Y_2) - \underbrace{V_b \cdot Y_2}_{=0 \text{ because } V_b = 0}$$



$$I_{s1}' = E_1 \cdot Y_1$$

$$E_1 \cdot Y_1 - I_{s2} = V_a \cdot (Y_1 + Y_2)$$

$$V_a = \frac{E_1 \cdot Y_1 - I_{s2}}{Y_1 + Y_2}$$

$$V_a = \frac{100 \cdot (-j) - (-j \cdot 10)}{1 - j}$$

$$V_a = \frac{-100j + 10j}{1 - j}$$

$$V_a = \frac{-90j \cdot (1 + j)}{(1 - j)(1 + j)} = \frac{-90j + 90}{-1 + j - j + 1}$$

$$V_a = 45 - 45j$$

$$J_1 + I_{s1}' - J_1' = 0$$



$$J_1 = J_1' - I_{s1}'$$

$$J_1 = (V_a - V_b) \cdot Y_1 - E_1 \cdot Y_1$$

$$J_2 = (V_a - V_b) \cdot Y_2$$

Mesh analysis uses Kirchoff's voltage law (KVL). Mesh analysis does not see current sources. Physical current sources are transformed to virtual voltage source  $I_s \rightarrow E'$ . Currents between meshes are sum of meshes currents. Number of equations for the Kirchoff's voltage law is given by formula:  
 equations for KVL =  $m - (n - 1)$   
 $m - (n - 1) = 2 - (2 - 1) = 1$
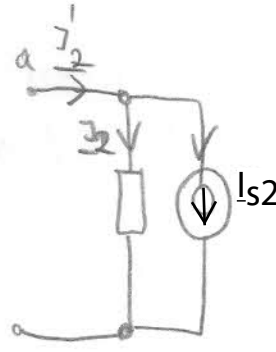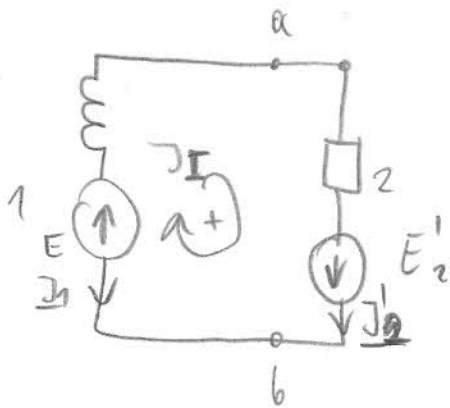
$$\left(\sum E\right)_I = E_1 + I_{s2} \cdot Z_2 = I_I (Z_1 + Z_2)$$



$$I_1 = -I_I$$

$$I_2' - I_2 - I_{s2} = 0$$

$$I_2 = I_2' - I_{s2}$$

$$I_2 = I_I - I_{s2}$$

$$I_I (Z_1 + Z_2) = E_1 + I_{s2} \cdot Z_2$$

$$I_I = \frac{E_1 + I_{s2} \cdot Z_2}{Z_1 + Z_2}$$

$$I_I = \frac{100 + (-j \cdot 10)}{1 + j}$$

$$I_I = \frac{(100 - 10j) \cdot (1 - j)}{(1 + j)(1 - j)}$$

$$I_I = \frac{100 - 100j - 10j - 10}{1 - j + j + 1}$$

$$I_I = \frac{90 - 110j}{2}$$

$$I_I = 45 - 55j$$