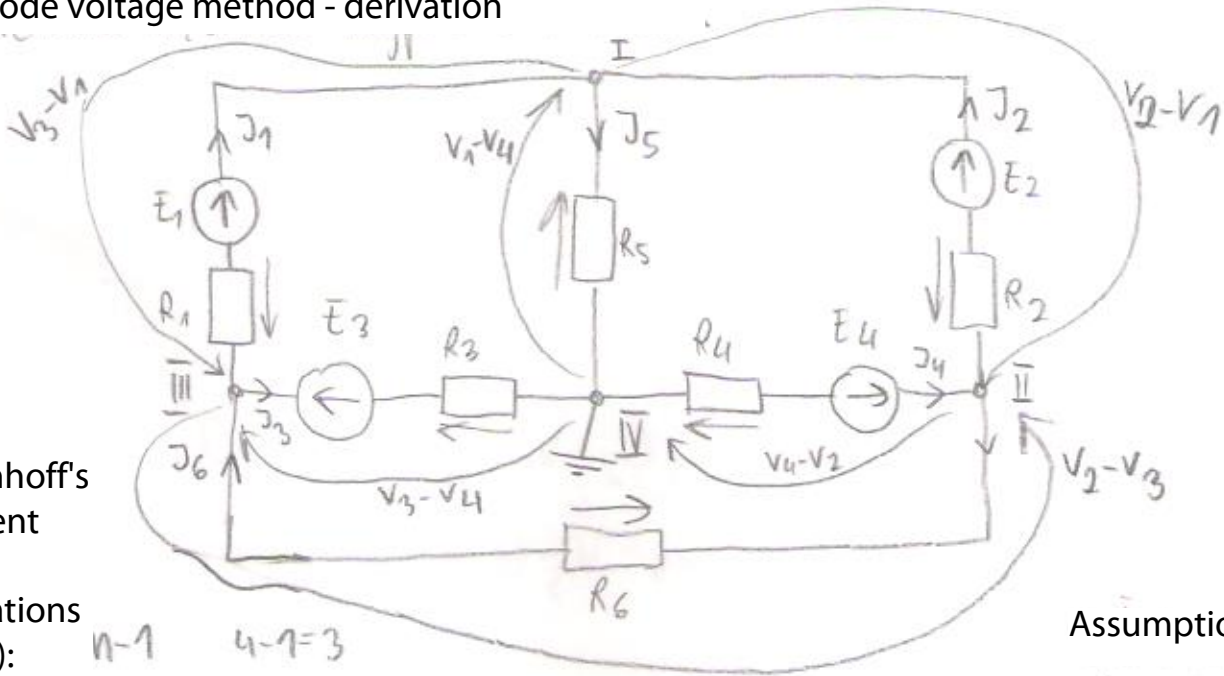


Node voltage method - derivation



Kirchhoff's current law equations (KCL):

Node I: $J_1 + J_2 - J_5 = 0$

Node II: $J_4 - J_2 - J_6 = 0$

Node III: $J_6 - J_3 - J_1 = 0$

Assumption: $V_4 = 0$

Kirchhoff's voltage law (KVL) equations for each branch separately:

$$(V_3 - V_1) - J_1 R_1 + E_1 = 0 \Rightarrow J_1 = \frac{(V_3 - V_1) + E_1}{R_1} \Rightarrow J_1 = (V_3 - V_1) \cdot G_1 + E_1 \cdot G_1$$

$$(V_2 - V_1) - J_2 R_2 + E_2 = 0 \Rightarrow J_2 = \frac{(V_2 - V_1) + E_2}{R_2} \Rightarrow J_2 = (V_2 - V_1) \cdot G_2 + E_2 \cdot G_2$$


$$(V_1 - V_4) - J_5 R_5 = 0 \Rightarrow J_5 = \frac{(V_1 - V_4)}{R_5} \Rightarrow J_5 = (V_1 - V_4) \cdot G_5$$

$$(V_3 - V_4) - E_3 - J_3 R_3 = 0 \Rightarrow J_3 = \frac{(V_3 - V_4) - E_3}{R_3} \Rightarrow J_3 = (V_3 - V_4) \cdot G_3 - E_3 \cdot G_3$$

$$(V_4 - V_2) - J_4 R_4 + E_4 = 0 \Rightarrow J_4 = \frac{(V_4 - V_2) + E_4}{R_4} \Rightarrow J_4 = (V_4 - V_2) \cdot G_4 + E_4 \cdot G_4$$

$$(V_2 - V_3) - J_6 R_6 = 0 \Rightarrow J_6 = \frac{(V_2 - V_3)}{R_6} \Rightarrow J_6 = (V_2 - V_3) \cdot G_6$$

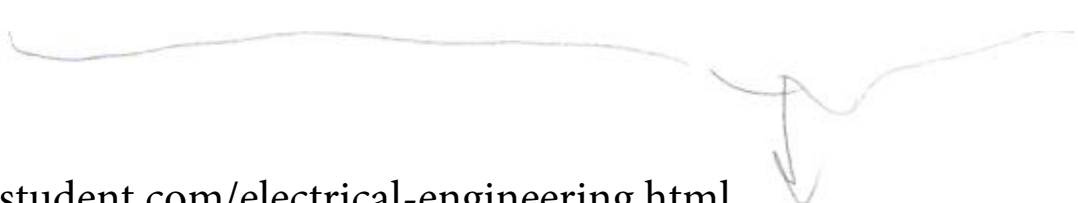Currents expressed by equations above are inserted to Kirchhoff's current law (KCL) equations:



$$(V_3 - V_1) \cdot G_1 + E_1 \cdot G_1 + (V_2 - V_1) \cdot G_2 + E_2 \cdot G_2 - (V_1 - V_4) \cdot G_5 = 0 \quad \text{Node I}$$

$$(V_4 - V_2) \cdot G_4 + E_4 \cdot G_4 - (V_2 - V_1) \cdot G_2 - E_2 \cdot G_2 - (V_2 - V_3) \cdot G_6 = 0 \quad \text{Node II}$$

$$(V_2 - V_3) \cdot G_6 - (V_3 - V_4) \cdot G_3 + E_3 \cdot G_3 - (V_3 - V_1) \cdot G_1 - E_1 \cdot G_1 = 0 \quad \text{Node III}$$

$$V_3 \cdot G_3 - V_1 \cdot G_1 + E_1 \cdot G_1 + V_2 \cdot G_2 - V_1 \cdot G_2 + E_2 \cdot G_2 - V_1 \cdot G_5 + V_4 \cdot G_5 = 0$$

$$V_4 \cdot G_4 - V_2 \cdot G_4 + E_4 \cdot G_4 - V_2 \cdot G_2 + V_1 \cdot G_2 - E_2 \cdot G_2 - V_2 \cdot G_6 + V_3 \cdot G_6 = 0$$

$$V_2 \cdot G_6 - V_3 \cdot G_6 - V_3 \cdot G_3 + V_4 \cdot G_3 + E_3 \cdot G_3 - V_3 \cdot G_1 + V_1 \cdot G_1 - E_1 \cdot G_1 = 0$$

Assumption: $V_4 = 0$

Counteractions

$$E_1 \cdot G_1 + E_2 \cdot G_2 = V_1(G_1 + G_2 + G_5) - \underbrace{V_3 \cdot G_1 - V_2 \cdot G_2 - V_4 \cdot G_5}_{=0 \text{ because } V_4=0}$$

$$E_4 \cdot G_4 - E_2 \cdot G_2 = V_2(G_2 + G_4 + G_6) - V_1 \cdot G_2 - V_3 \cdot G_6 - \underbrace{V_4 \cdot G_4}_{=0 \text{ because } V_4=0}$$

$$E_3 \cdot G_3 - E_1 \cdot G_1 = V_3(G_1 + G_2 + G_6) - V_1 \cdot G_1 - V_2 \cdot G_6 - \underbrace{V_4 \cdot G_3}_{=0 \text{ because } V_4=0}$$

Node's own conductances

Conductances of nodes which are in counteraction

$$\left(\sum J_s \right)_{\text{I}} = E_1 \cdot G_1 + E_2 \cdot G_2 = V_1(G_1 + G_2 + G_5) - \underbrace{V_2 \cdot G_2 - V_3 \cdot G_1 - V_4 \cdot G_5}_{=0, \rightarrow V_4=0}$$

$$\left(\sum J_s \right)_{\text{II}} = E_4 \cdot G_4 - E_2 \cdot G_2 = V_2(G_2 + G_4 + G_6) - V_1 \cdot G_2 - V_3 \cdot G_6 - \underbrace{V_4 \cdot G_4}_{=0, \rightarrow V_4=0}$$

$$\left(\sum J_s \right)_{\text{III}} = E_3 \cdot G_3 - E_1 \cdot G_1 = V_3(G_1 + G_3 + G_6) - V_1 \cdot G_1 - V_2 \cdot G_6 - \underbrace{V_4 \cdot G_3}_{=0, \rightarrow V_4=0}$$